

SPARTAN6 - DSP48A1 PROJECT

USING FPGA DESIGN FLOW

Marwan Khaled Mohamed

Contents

1	Project specifications	4
1.1	Input – output ports	4
1.2	Schematic – internal signals	5
2	Code	6
2.1	Design code	6
2.1.1	Basic block code	6
2.1.2	Top module Code	7
2.2	Testbench	9
3	Do File	11
4	Waveform	11
4.1	Waveform for input – output ports	11
4.2	Waveform for internal signals	12
5	Vivado Design Flow	12
5.1	Elaboration	12
5.2	Time constraints	13
5.3	Synthesis	13
5.3.1	Synthesis Schematic	13
5.3.2	Detailed Schematic	14
5.3.3	Synthesis Timing Report	15
5.3.4	Synthesis Utilization Report	15
5.4	Implementation	16
5.4.1	Implementation Device	16
5.4.2	Implementation Timing Report	17
5.4.3	Implementation Utilization Report	17
6	Message Tab	18
6.1	Message Tab for elaborated design	18
6.2	Message Tab for Synthesized design	18
6.3	Message Tab for implemented design	18

Figure 1: input output port	4
Figure 2 Schematic modified with the name of internal signals	5
Figure 3: Basic Block Code	6
Figure 4: Design Code Part1	7
Figure 5: Design Code Part2	8
Figure 6: Design Code Part3	8
Figure 7: Testbench Part1.....	9
Figure 8: Testbench Part2.....	10
Figure 9: Testbench Part3.....	10
Figure 10: Do file	11
Figure 11: Waveform of input- Output Port.....	11
Figure 12: Waveform of internal Signals in the Design	12
Figure 13: Elaborated Design Schematic.....	12
Figure 14: Time constraints File	13
Figure 15: Synthesis Schematic.....	13
Figure 16: DSP48E1 block in FPGA used to Synthesis the Design	14
Figure 17: Timing report in synthesis stage	15
Figure 18: Utilization report in synthesis stage.....	15
Figure 19: Design implemented on FPGA	16
Figure 20: Timing report in implementation stage	17
Figure 21: Utilization report in implementation stage.....	17
Figure 22: Message Tab for elaborated design	18
Figure 23 : Message Tab for Synthesized design.....	18
Figure 24: Message Tab for implemented design	18

1 Project specifications

1.1 Input – output ports

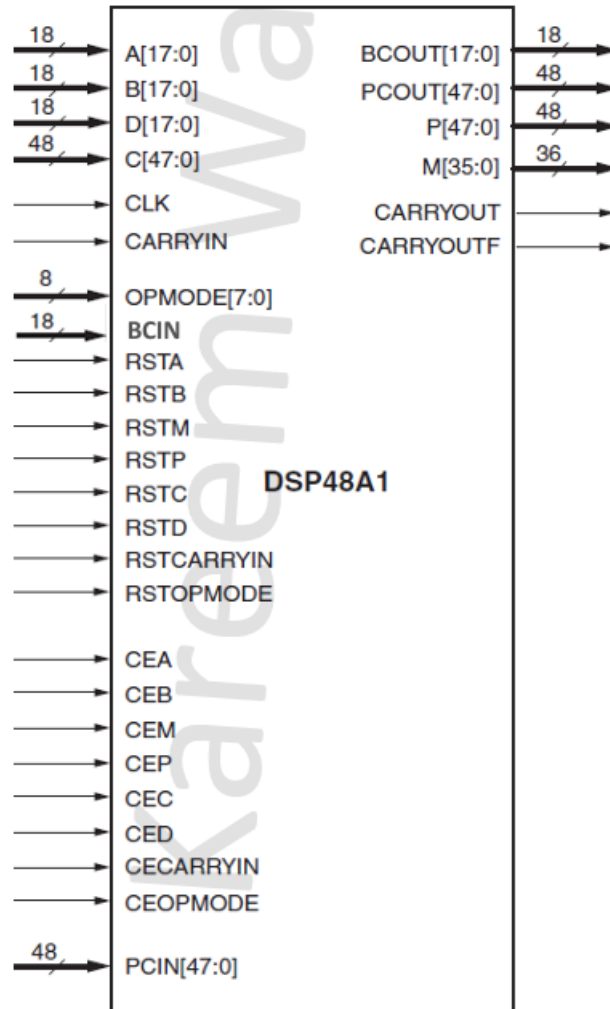


Figure 1: input output port

1.2 Schematic – internal signals

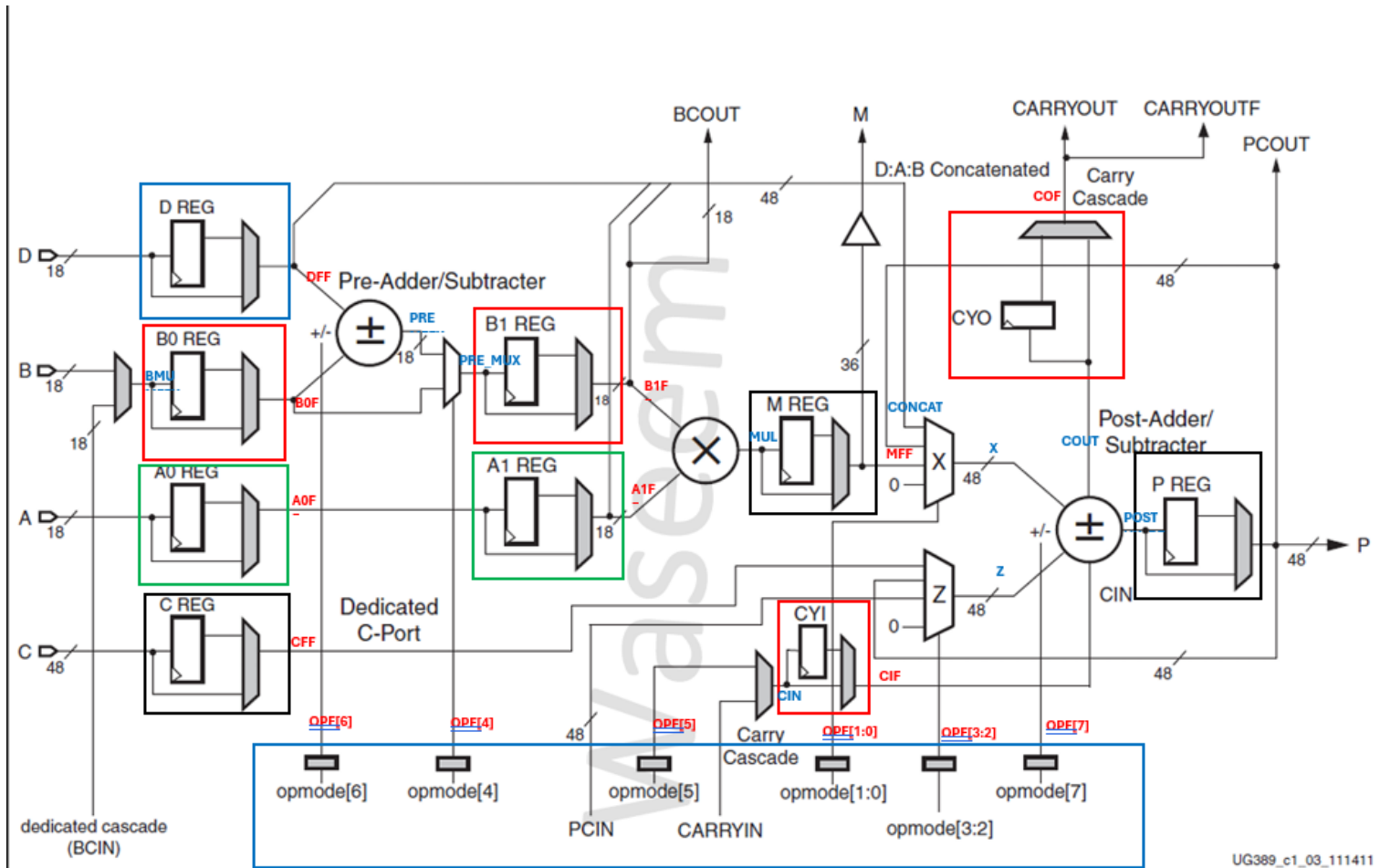


Figure 2 Schematic modified with the name of internal signals

UG389_c1_03_111411

2 Code

2.1 Design code

2.1.1 Basic block code

```

module MUX_REGISTER(the_input,clk,CE,rst,the_output);
parameter width=18;
parameter selection=1;
parameter RSTTYPE="SYNC";
input [width-1:0] the_input;
input clk,rst,CE;
output reg [width-1:0] the_output;

generate
    if(selection==1)
    begin
        if(RSTTYPE=="SYNC")
        begin
            always @(posedge clk ) begin
                if (rst)
                    the_output<=0;
                else if(CE==1)
                    the_output<=the_input;
            end
        end
        else if(RSTTYPE=="ASYNC") begin
            always @(posedge clk or posedge rst ) begin
                if (rst)
                    the_output<=0;
                else if(CE==1)
                    the_output<=the_input;
            end
        end
    end
    else if(selection==0)
    begin
        always @(the_input ) begin
            the_output=the_input;
        end
    end
endgenerate
endmodule

```

Figure 3: Basic Block Code

2.1.2 Top module Code

```

1  module DSP(A,B,C,D,CARRYIN,M,P,CARRYOUT,CARRYOUTF,CLK,OPMODE,CEA,CEB,CECARRYIN,CEC,CED,CEM,CEOPMODE
2  ,CEP,RSTA,RSTB,RSTC,RSTCARRYIN,RSTD,RSTM,RSTP,RSTOPMODE,BCOUT,PCIN,BCIN,PCOUT);
3
4  input [17:0] A,B,D,BCIN;
5  input [47:0] C,PCIN;
6  input [7:0] OPMODE;
7  input CARRYIN,CLK,CEA,CEB,CECARRYIN,CEC,CED,CEM,CEOPMODE,CEP,RSTA,RSTB,RSTC,RSTCARRYIN,RSTD,RSTM,RSTP,RSTOPMODE;
8  output CARRYOUTF,CARRYOUT;
9  output [47:0] PCOUT,P;
10 output [17:0] BCOUT;
11 output [35:0] M;
12 /*.....parameter.....*/
13 parameter A0REG=0;
14 parameter A1REG=1;
15
16 parameter B0REG=0;
17 parameter B1REG=1;
18
19 parameter CREG=1;
20 parameter DREG=1;
21 parameter MREG=1;
22 parameter PREG=1;
23 parameter CARRYINREG=1;
24 parameter CARRYOUTREG=1;
25 parameter OPMODEREG=1;
26
27 parameter CARRYINSEL="OPMODE5"; //CARRYIN
28 parameter B_INPUT="DIRECT"; //CASCADE
29 parameter RSTTYPE="SYNC"; //ASYNC
30 /*..... instances wires..... */
31 wire [17:0] DFF,B0F,A0F,B1F,A1F;
32 wire [47:0] CFF;

```

Figure 4: Design Code Part1

```

33 wire [35:0] MFF;
34 wire CIF,COF;
35 wire [7:0] OPF;
36 wire [17:0] BMUX;
37
38 /*.....internal signals .....*/
39 wire [17:0] PRE_MUX,PRE;
40 wire [35:0] MUL;
41 wire [47:0] POST;
42 wire [47:0] X,Z;
43 wire [47:0] CONCAT;
44 wire COUT,CIN;
45 /*..... FIRST STAGE .....*/
46 MUX_REGISTER #(.width(18),.selection(DREG)) DUT_DREG(D,CLK,CED,RSTD,DFF);
47
48 assign BMUX=(B_INPUT=="DIRECT")? B:(B_INPUT=="CASCADE")?PCIN:0 ;
49 MUX_REGISTER #(.width(18),.selection(B0REG)) DUT_B0REG(BMUX,CLK,CEB,RSTB,B0F);
50
51 MUX_REGISTER #(.width(18),.selection(A0REG)) DUT_A0REG(A,CLK,CEA,RSTA,A0F);
52
53 MUX_REGISTER #(.width(48),.selection(CREG)) DUT_CREG(C,CLK,CEC,RSTC,CFF);
54
55 MUX_REGISTER #(.width(8),.selection(OPMODEREG)) DUT_OPMODEREG(OPMODE,CLK,CEOPMODE,RSTOPMODE,OPF);
56
57 /*..... SECOND STAGE .....*/
58 MUX_REGISTER #(.width(18),.selection(B1REG)) DUT_B1REG(PRE_MUX,CLK,CEB,RSTB,B1F);
59
60 MUX_REGISTER #(.width(18),.selection(A0REG)) DUT_A1REG(A0F,CLK,CEA,RSTA,A1F);
61
62 /*..... THIRD STAGE .....*/
63 MUX_REGISTER #(.width(36),.selection(MREG)) DUT_MREG(MUL,CLK,CEM,RSTM,MFF);
64

```

Figure 5: Design Code Part2

```

65 /*..... FOURTH STAGE .....*/
66 MUX_REGISTER #(.width(48),.selection(PREG)) DUT_PREG(POST,CLK,CEP,RSTP,P);
67 MUX_REGISTER #(.width(1),.selection(CARRYOUTREG)) DUT_COREG(COUT,CLK,CECARRYIN,RSTCARRYIN,COF);
68 MUX_REGISTER #(.width(1),.selection(CARRYINREG)) DUT_CINREG(CIN,CLK,CECARRYIN,RSTCARRYIN,CIF);
69
70 /*..... Calculate the internal signal.....*/
71
72 assign CIN=(CARRYINSEL=="OPMODES")? OPMODE[5]:(CARRYINSEL=="CARRYIN")? CARRYIN:0;
73 assign MUL=A1F*B1F;
74 assign BCOUT=B1F;
75 assign M=MFF;
76 assign CONCAT={DFF[12:0],A1F,B1F};
77 assign CARRYOUT=COF;
78 assign CARRYOUTF=COF;
79 assign PCOUT=P;
80 assign PRE=(OPMODE[6]==0)? (DFF+B0F):(DFF-B0F) ;
81 assign PRE_MUX=(OPMODE[4]==0) ? B0F:PRE;
82 assign X={({OPMODE[1],OPMODE[0]}==2'b00)? 0: ({OPMODE[1],OPMODE[0]}==2'b01)? ({12'b000000000000,MFF}):({OPMODE[1],OPMODE[0]}==2'b10)?P:CONCAT;
83 assign Z={({OPMODE[3],OPMODE[2]}==2'b00)? 0: ({OPMODE[3],OPMODE[2]}==2'b01)? PCIN:({OPMODE[3],OPMODE[2]}==2'b10)?P:CFF;
84 assign {COUT,POST}=(OPMODE[7]==0)? (Z+X+CIF):(Z-(X+CIF));
85
86 endmodule

```

Figure 6: Design Code Part3

2.2 Testbench

```

1  module DSP_tb();
2
3  reg [17:0] A_tb,B_tb,D_tb,BCIN_tb;
4  reg [47:0] C_tb,PCIN_tb;
5  reg [7:0] OPMODE_tb;
6  reg CARRYIN_tb,CLK_tb,CEA_tb,CEB_tb,CECARRYIN_tb,CEC_tb,CED_tb,CEM_tb,CEOPMODE_tb,CEP_tb;
7  reg RSTA_tb,RSTB_tb,RSTC_tb,RSTCARRYIN_tb,RSTD_tb,RSTM_tb,RSTP_tb,RSTOPMODE_tb;
8  wire CARRYOUTF,CARRYOUT;
9  wire [47:0] PCOUT,P;
10 wire [17:0] BCOUT;
11 wire [35:0] M;
12 DSP DUT(A_tb,B_tb,C_tb,D_tb,CARRYIN_tb,M,P,CARRYOUT,CARRYOUTF,CLK_tb,OPMODE_tb,CEA_tb,CEB_tb,CECARRYIN_tb,CEC_tb,CED_tb,CEM_tb,CEOPMODE_tb
13 ,CEP_tb,RSTA_tb,RSTB_tb,RSTC_tb,RSTCARRYIN_tb,RSTD_tb,RSTM_tb,RSTP_tb,RSTOPMODE_tb,BCOUT,PCIN_tb,BCIN_tb,PCOUT);
14 integer i;
15 initial begin
16   CLK_tb=0;
17   forever
18     #4 CLK_tb=~CLK_tb;
19   end
20
21   initial begin
22     CEA_tb=1;CEB_tb=1;CECARRYIN_tb=1; CEC_tb=1;CED_tb=1;CEM_tb=1;CEOPMODE_tb=1;CEP_tb=1;
23     RSTA_tb=0;RSTB_tb=0;RSTC_tb=0;RSTCARRYIN_tb=0;RSTD_tb=0;RSTM_tb=0;RSTP_tb=0;RSTOPMODE_tb=0;
24
25     /* (D+B)*A+C+CIN */ /* 23 */
26     A_tb=2; B_tb=3; C_tb=4; D_tb=6; PCIN_tb=2; CARRYIN_tb=1; BCIN_tb=0;
27     OPMODE_tb[1]=0; OPMODE_tb[0]=1; OPMODE_tb[3]=1; OPMODE_tb[2]=1; OPMODE_tb[4]=1; OPMODE_tb[5]=1; OPMODE_tb[6]=0; OPMODE_tb[7]=0;
28     for(i=0;i<4;i=i+1)
29       @(negedge CLK_tb);
30
31     /* (D+B)*A+CIN */ /* 10 */
32     A_tb=3; B_tb=1; C_tb=5; D_tb=2; PCIN_tb=2; CARRYIN_tb=1; BCIN_tb=0;
33     OPMODE_tb[1]=0; OPMODE_tb[0]=1; OPMODE_tb[3]=0; OPMODE_tb[2]=0; OPMODE_tb[4]=1; OPMODE_tb[5]=1; OPMODE_tb[6]=0; OPMODE_tb[7]=0;
34     for(i=0;i<4;i=i+1)
35       @(negedge CLK_tb);

```

Figure 7: Testbench Part1

```

36
37 /* (D-B)*A+CIN*/ /* 57 */
38 A_tb=4; B_tb=1; C_tb=6; D_tb=15; PCIN_tb=2; CARRYIN_tb=1; BCIN_tb=0;
39 OPMODE_tb[1]=0; OPMODE_tb[0]=1; OPMODE_tb[3]=0; OPMODE_tb[2]=0; OPMODE_tb[4]=1; OPMODE_tb[5]=1; OPMODE_tb[6]=1; OPMODE_tb[7]=0;
40 for(i=0;i<4;i=i+1)
41 @(negedge CLK_tb);
42
43 /* (D-B)*A+C+CIN */ /* 268 */
44 A_tb=5; B_tb=8; C_tb=7; D_tb=60; PCIN_tb=2; CARRYIN_tb=1; BCIN_tb=0;
45 OPMODE_tb[1]=0; OPMODE_tb[0]=1; OPMODE_tb[3]=1; OPMODE_tb[2]=1; OPMODE_tb[4]=1; OPMODE_tb[5]=1; OPMODE_tb[6]=1; OPMODE_tb[7]=0;
46 for(i=0;i<4;i=i+1)
47 @(negedge CLK_tb);
48
49 /* B*A+CIN*/ /* 10 */
50 A_tb=1; B_tb=9; C_tb=1; D_tb=5; PCIN_tb=2; CARRYIN_tb=1; BCIN_tb=0;
51 OPMODE_tb[1]=0; OPMODE_tb[0]=1; OPMODE_tb[3]=0; OPMODE_tb[2]=0; OPMODE_tb[4]=0; OPMODE_tb[5]=1; OPMODE_tb[6]=0; OPMODE_tb[7]=0;
52 for(i=0;i<4;i=i+1)
53 @(negedge CLK_tb);
54
55 /* (B*A)+C+CIN */ /* 7 */
56 A_tb=4; B_tb=1; C_tb=2; D_tb=1; PCIN_tb=2; CARRYIN_tb=1; BCIN_tb=0;
57 OPMODE_tb[1]=0; OPMODE_tb[0]=1; OPMODE_tb[3]=1; OPMODE_tb[2]=1; OPMODE_tb[4]=0; OPMODE_tb[5]=1; OPMODE_tb[6]=0; OPMODE_tb[7]=0;
58 for(i=0;i<4;i=i+1)
59 @(negedge CLK_tb);
60
61 /* C+CIN*/ /* 5 */
62 A_tb=1; B_tb=3; C_tb=4; D_tb=2; PCIN_tb=2; CARRYIN_tb=1; BCIN_tb=0;
63 OPMODE_tb[1]=0; OPMODE_tb[0]=0; OPMODE_tb[3]=1; OPMODE_tb[2]=1; OPMODE_tb[4]=1; OPMODE_tb[5]=1; OPMODE_tb[6]=0; OPMODE_tb[7]=0;
64 for(i=0;i<4;i=i+1)
65 @(negedge CLK_tb);
66
67 /* CIN */ /* 1 */
68 A_tb=2; B_tb=10; C_tb=5; D_tb=4; PCIN_tb=1; CARRYIN_tb=1; BCIN_tb=0;
69 OPMODE_tb[1]=0; OPMODE_tb[0]=0; OPMODE_tb[3]=0; OPMODE_tb[2]=0; OPMODE_tb[4]=1; OPMODE_tb[5]=1; OPMODE_tb[6]=0; OPMODE_tb[7]=0;
70 for(i=0;i<4;i=i+1)

```

Figure 8: Testbench Part2

```

71 @(negedge CLK_tb);
72
73 /* PCIN+CIN */ /* 5 */
74 A_tb=7; B_tb=3; C_tb=4; D_tb=1; PCIN_tb=4; CARRYIN_tb=1; BCIN_tb=0;
75 OPMODE_tb[1]=0; OPMODE_tb[0]=0; OPMODE_tb[3]=0; OPMODE_tb[2]=1; OPMODE_tb[4]=1; OPMODE_tb[5]=1; OPMODE_tb[6]=0; OPMODE_tb[7]=0;
76 for(i=0;i<4;i=i+1)
77 @(negedge CLK_tb);
78
79 /* P+CIN */ /* 6 ,7 , 8, 9 */
80 A_tb=2; B_tb=3; C_tb=2; D_tb=6; PCIN_tb=2; CARRYIN_tb=1; BCIN_tb=0;
81 OPMODE_tb[1]=1; OPMODE_tb[0]=0; OPMODE_tb[3]=0; OPMODE_tb[2]=0; OPMODE_tb[4]=1; OPMODE_tb[5]=1; OPMODE_tb[6]=0; OPMODE_tb[7]=0;
82 for(i=0;i<4;i=i+1)
83 @(negedge CLK_tb);
84
85 $stop;
86 end
87
88 endmodule

```

Figure 9: Testbench Part3

3 Do File

```
1 vlib work
2 vlog DSP.v DSP_tb.v
3 vsim -voptargs=+acc work.DSP_tb
4 add wave *
5 run -all
```

Figure 10: Do file

4 Waveform

4.1 Waveform for input – output ports



Figure 11: Waveform of input- Output Port

4.2 Waveform for internal signals

 


Figure 12: Waveform of internal Signals in the Design

5 Vivado Design Flow

5.1 Elaboration

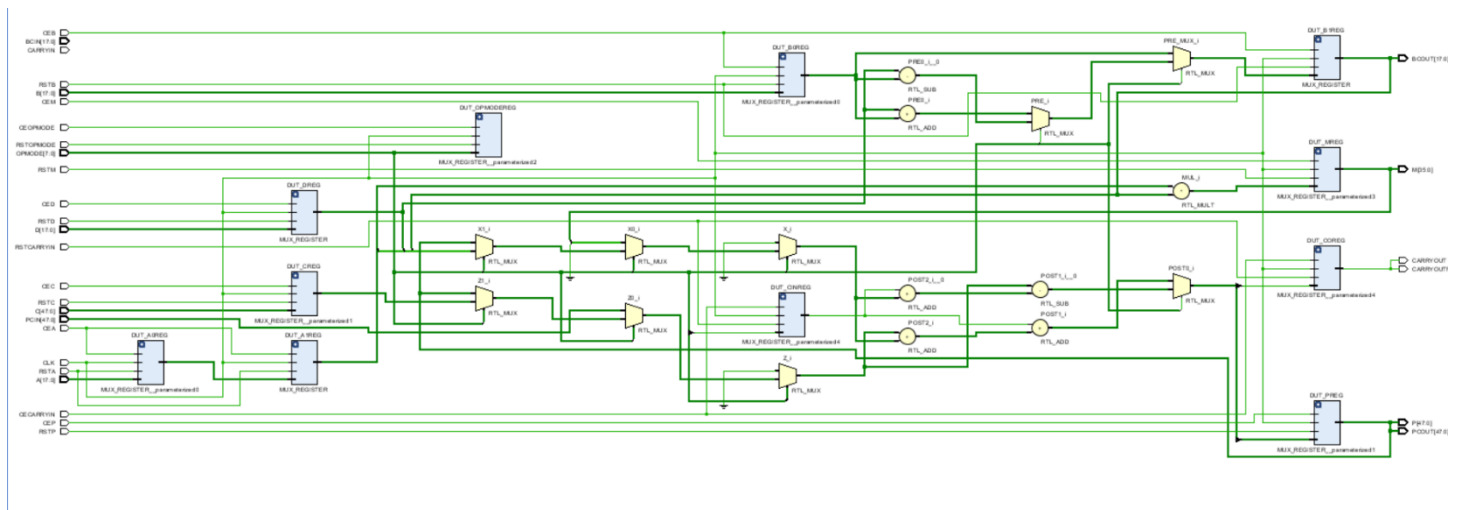


Figure 13: Elaborated Design Schematic

5.2 Time constraints

```
## Clock signal
set_property -dict {PACKAGE_PIN W5 IOSTANDARD LVCMOS33} [get_ports CLK]
create_clock -period 10.000 -name sys_clk_pin -waveform {0.000 5.000} -add [get_ports CLK]
```

Figure 14: Time constraints File

5.3 Synthesis

5.3.1 Synthesis Schematic

 


Figure 15: Synthesis Schematic

5.3.2 Detailed Schematic

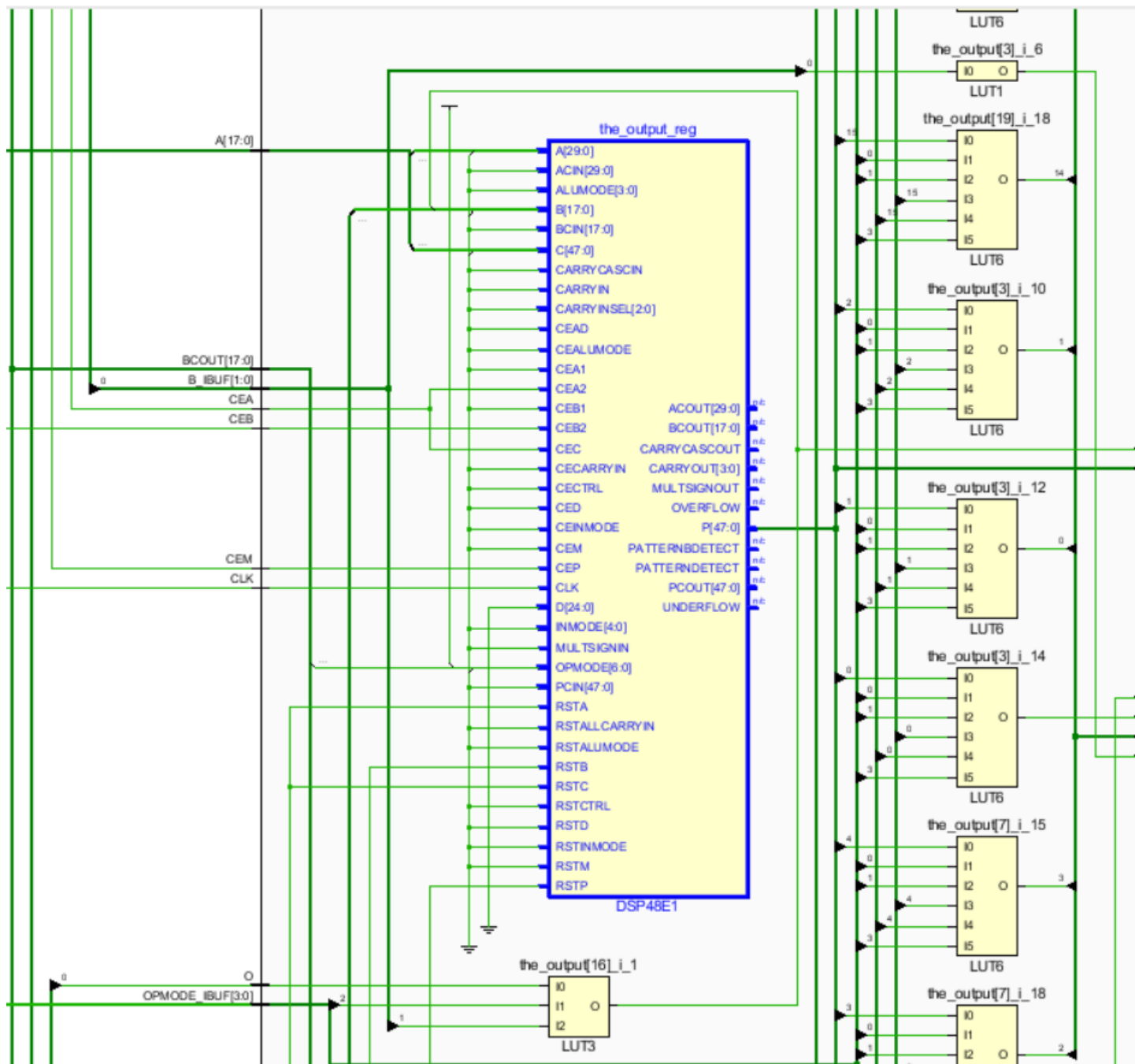


Figure 16: DSP48E1 block in FPGA used to Synthesis the Design

5.3.3 Synthesis Timing Report

Design Timing Summary					
Setup		Hold		Pulse Width	
Worst Negative Slack (WNS): 5.259 ns		Worst Hold Slack (WHS): 0.341 ns		Worst Pulse Width Slack (WPWS): 4.500 ns	
Total Negative Slack (TNS): 0.000 ns		Total Hold Slack (THS): 0.000 ns		Total Pulse Width Negative Slack (TPWS): 0.000 ns	
Number of Failing Endpoints: 0		Number of Failing Endpoints: 0		Number of Failing Endpoints: 0	
Total Number of Endpoints: 86		Total Number of Endpoints: 86		Total Number of Endpoints: 154	
All user specified timing constraints are met.					

Figure 17: Timing report in synthesis stage

5.3.4 Synthesis Utilization Report

Name	Slice LUTs (134600)	Slice Registers (269200)	DSP s (740)	Bonded IOB (500)	BUFGCTRL (32)
▼ N DSP	229	152	1	325	1
dbg_hub (dbg_hub_CV)	0	0	0	0	0
DUT_A1REG (MUX_R...	0	18	0	0	0
DUT_B1REG (MUX_R...	1	18	0	0	0
DUT_CINREG (MUX_...	0	1	0	0	0
DUT_COREG (MUX_R...	0	1	0	0	0
DUT_CREG (MUX_RE...	96	48	0	0	0
DUT_DREG (MUX_RE...	46	18	0	0	0
DUT_MREG (MUX_RE...	39	0	1	0	0
DUT_PREG (MUX_RE...	47	48	0	0	0
u_ila_0 (u_ila_0_CV)	0	0	0	0	0

Figure 18: Utilization report in synthesis stage

5.4 Implementation

5.4.1 Implementation Device

 


Figure 19: Design implemented on FPGA

5.4.2 Implementation Timing Report

Setup	Hold	Pulse Width
Worst Negative Slack (WNS): 2.895 ns	Worst Hold Slack (WHS): 0.057 ns	Worst Pulse Width Slack (WPWS): 3.950 ns
Total Negative Slack (TNS): 0.000 ns	Total Hold Slack (THS): 0.000 ns	Total Pulse Width Negative Slack (TPWS): 0.000 ns
Number of Failing Endpoints: 0	Number of Failing Endpoints: 0	Number of Failing Endpoints: 0
Total Number of Endpoints: 7672	Total Number of Endpoints: 7656	Total Number of Endpoints: 4881
All user specified timing constraints are met.		

Figure 20: Timing report in implementation stage

5.4.3 Implementation Utilization Report

Name	Slice LUTs (133800)	Slice Registers (267600)	F7 Muxes (66900)	F8 Muxes (33450)	Slice (33450)	LUT as Logic (133800)	LUT as Memory (46200)	LUT Flip Flop Pairs (133800)	Block RAM Tile (365)	DSP s (740)	Bonded IOB (500)	BUFCTRL (32)	BSCANE2 (4)
▼ DSP	2547	4018	96	7	1228	2099	448	1474	8	1	325	2	1
> dbg_hub (dbg_hub)	475	727	0	0	233	451	24	314	0	0	0	1	1
DUT_A1REG (MUX_R...	0	18	0	0	8	0	0	0	0	0	0	0	0
DUT_B1REG (MUX_R...	1	18	0	0	7	1	0	1	0	0	0	0	0
DUT_CINREG (MUX_...	0	1	0	0	1	0	0	0	0	0	0	0	0
DUT_COREG (MUX_R...	0	2	0	0	2	0	0	0	0	0	0	0	0
DUT_CREG (MUX_RE...	96	48	0	0	31	96	0	0	0	0	0	0	0
DUT_DREG (MUX_RE...	29	18	0	0	13	29	0	0	0	0	0	0	0
DUT_MREG (MUX_RE...	54	0	0	0	23	54	0	0	0	1	0	0	0
DUT_PREG (MUX_RE...	48	48	0	0	27	48	0	0	0	0	0	0	0
> u_ila_0 (u_ila_0)	1843	3138	96	7	936	1419	424	1101	8	0	0	0	0

Figure 21: Utilization report in implementation stage

6 Message Tab

6.1 Message Tab for elaborated design

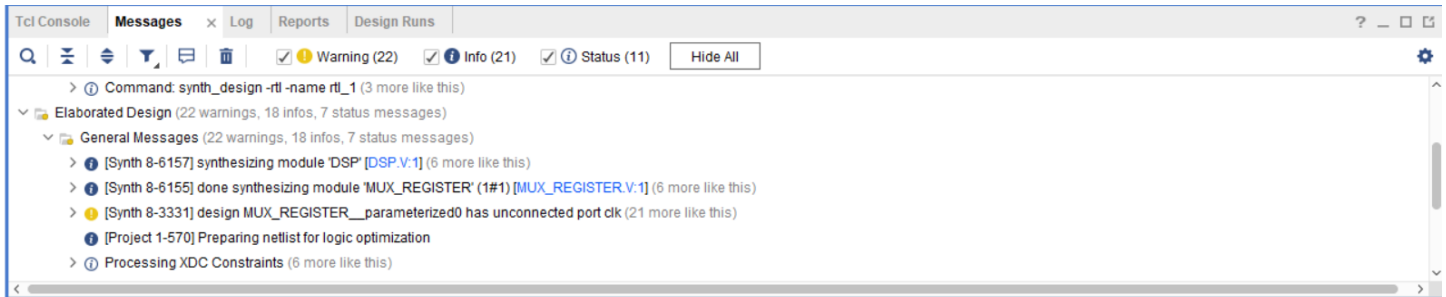


Figure 22: Message Tab for elaborated design

6.2 Message Tab for Synthesized design

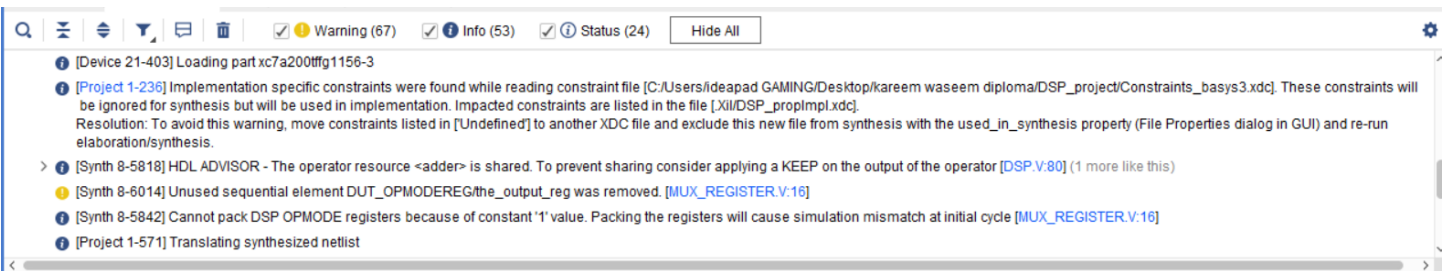


Figure 23 : Message Tab for Synthesized design

6.3 Message Tab for implemented design

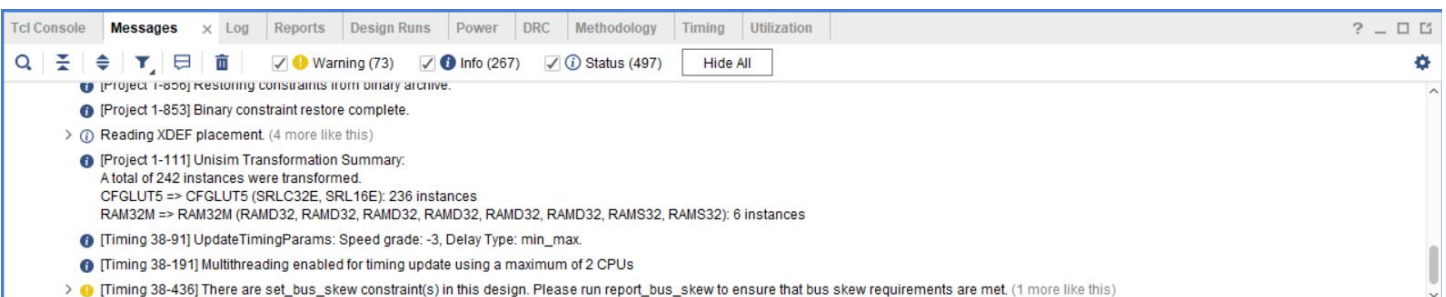


Figure 24: Message Tab for implemented design